

ARITHMETIC LOGIC UNIT OPERATIONS  
(ALU using 4-bit microprocessor)

Dhruvi Shah DDS200004

Navya Bandari NXB210004


Naga Mutya Kumar Kumtsam NXK210028




## Description

The project is to design and simulate arithmetic logic unit operations using 4-bit microprocessor.

## Block Diagram of Design

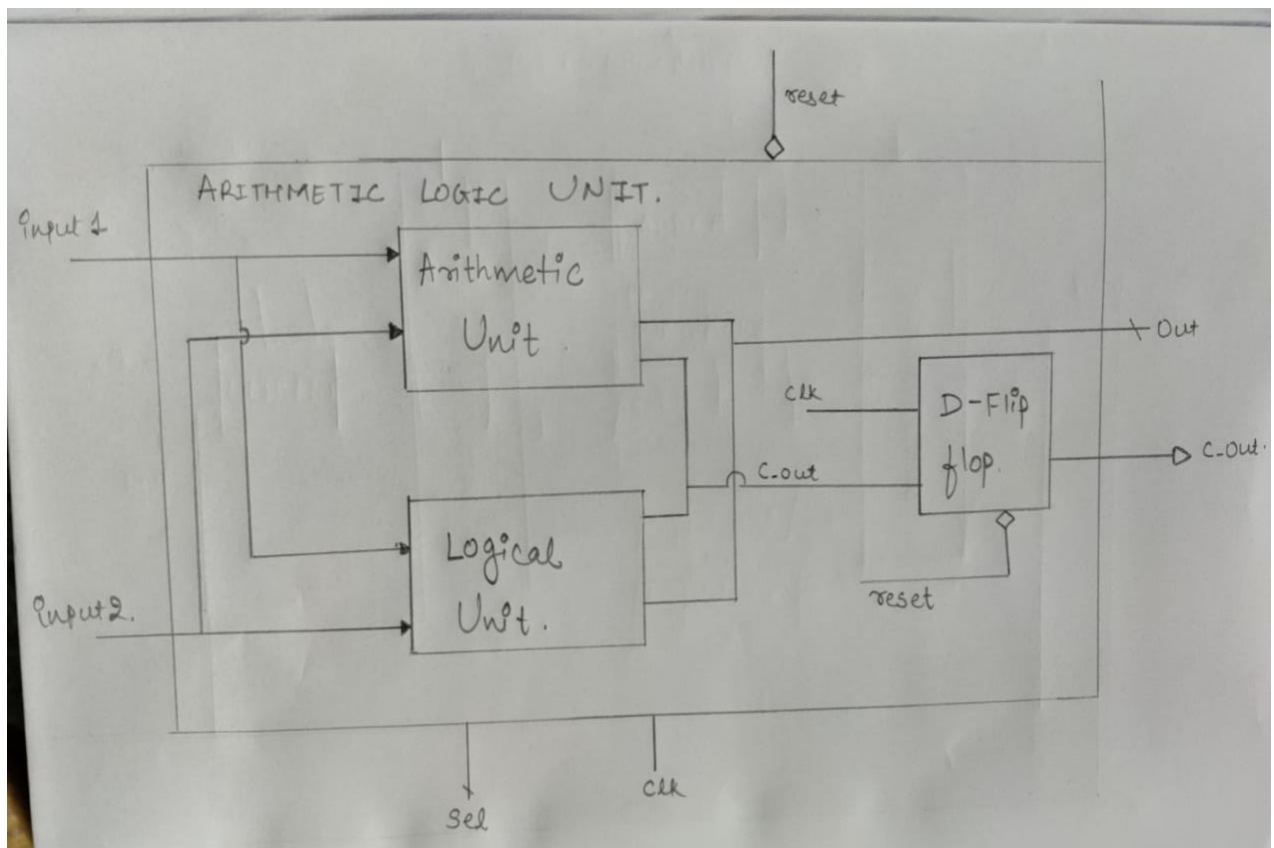
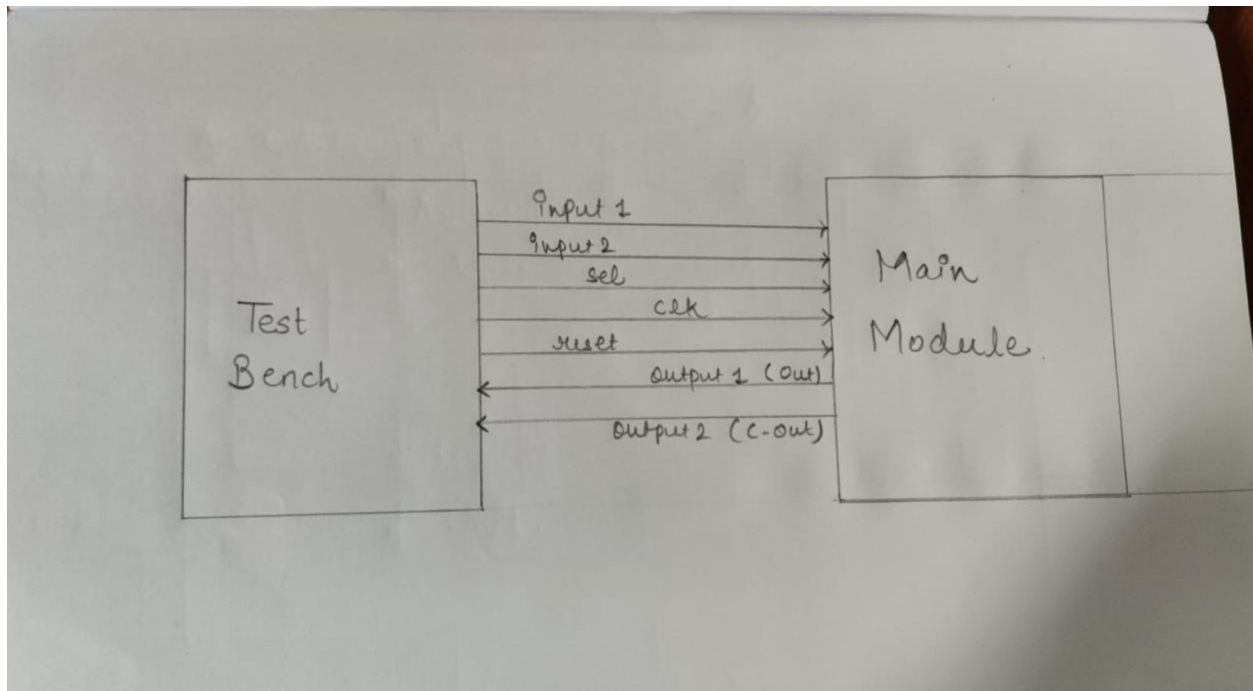
## Connection between Test bench and Module



## VERILOG CODE:

```
module MAIN(input1,input2,reset,clk,sel,out,c_out);
input[7:0] input1,input2;
input reset;
input clk;
input[3:0] sel;
output[7:0] out;
output c_out;
reg[7:0] out;
reg c_out;
always@(posedge clk)
begin
    //Implementing D-FlipFlop. If the reset signal is 1,c_out will be reset
    if(reset)
        c_out = 1'b0;
    else
        begin
            case(sel)
                // Arithmetic Addition
                4'b0000: begin {c_out,out} = input1 + input2; end
                //Arithmetic Subtraction
                4'b0001: begin {c_out,out} = input1 - input2; end
```

```

        //Logical AND Operation. 'c_out' is not used so it is
initialised as 0
        4'b0010: begin out = input1 & input2; c_out = 1'b0;
end

        //Logical OR Operation. 'c_out' is not used so it is
initialised as 0
        4'b0011: begin out = input1 | input2; c_out = 1'b0; end
        //Logical shift left Operation. 'c_out' is initialised as 0
        4'b0100: begin out = input1<<1; c_out = 1'b0; end
        //Logical Shift right 'c_out' is initialised as 0
        4'b0101: begin out = input1>> 1; c_out = 1'b0; end
        // Comparison Operations where 'out' is not used to
initialised to 8'd0
        4'b0110: begin c_out = (input1>input2) ? 1'b1:1'b0; out
= 8'd0; end
        4'b0111: begin c_out = (input1<input2) ? 1'b1:1'b0; out
= 8'd0;end
        4'b1000: begin c_out = (input1==input2) ? 1'b1:1'b0;
out = 8'd0; end
        endcase
    end
end
endmodule

```

### TEST BENCH CODE:

```
module MAIN_TB;
reg[7:0] input1,input2;
reg clk,reset;
reg[3:0] sel;

wire[7:0] out;
wire c_out;

MAIN DUT(input1,input2,reset,clk,sel,out,c_out);

initial begin
    #0 input1 = 8'd250; input2 = 8'd200;
    #0 sel = 4'b0010;
    reset = 0;
    clk =0;
end
always begin
    #30 clk = !clk;
end
endmodule
```

## SIMULATION WAVEFORM OUTPUT:

### Addition:

input 1: (250)=11111010

input 2: (200)=11001000


sel: (0000)

reset : 0

clk : 1

out :input1+input2=11000010

c\_out: 1

 

## Subtraction:

input 1: (250)=11111010

input 2: (200)=11001000


sel: (0001)

reset : 0

clk : 0

out :input1-input2=11000010

c\_out: 1

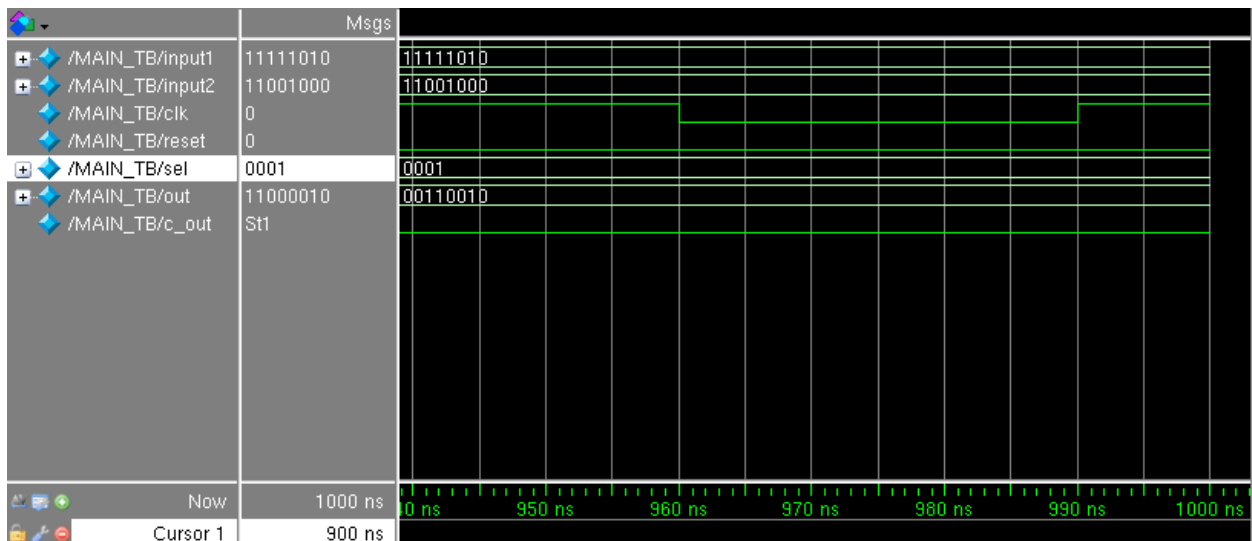



## Logical AND:

input 1: (250)=11111010

input 2: (200)=11001000


sel: (0010)

reset : 0

clk : 1

out :input1&input2=11001000

c\_out: 0

 

## Logical OR:

input 1: (250)=11111010

input 2: (200)=11001000


sel: (0011)

reset : 0

clk : 0

out :input1 | input2=11111010

c\_out: 0

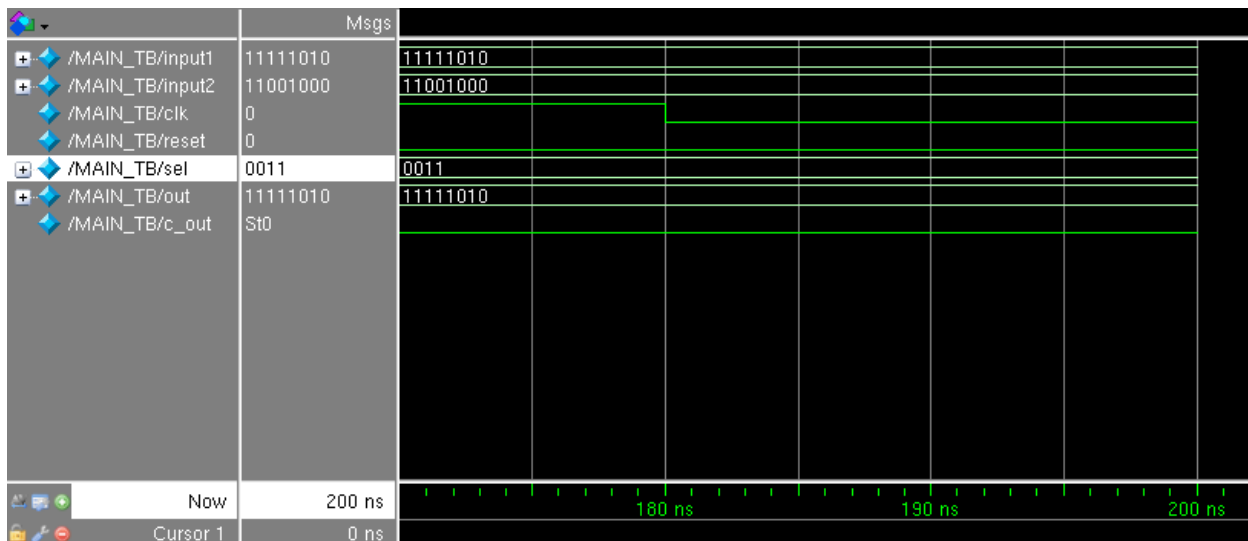

## Shift left:

input 1: (250)=11111010

input 2: (200)=11001000


sel: (0100)

reset : 0

clk : 0

out :input1<<1=11110100

c\_out: 0

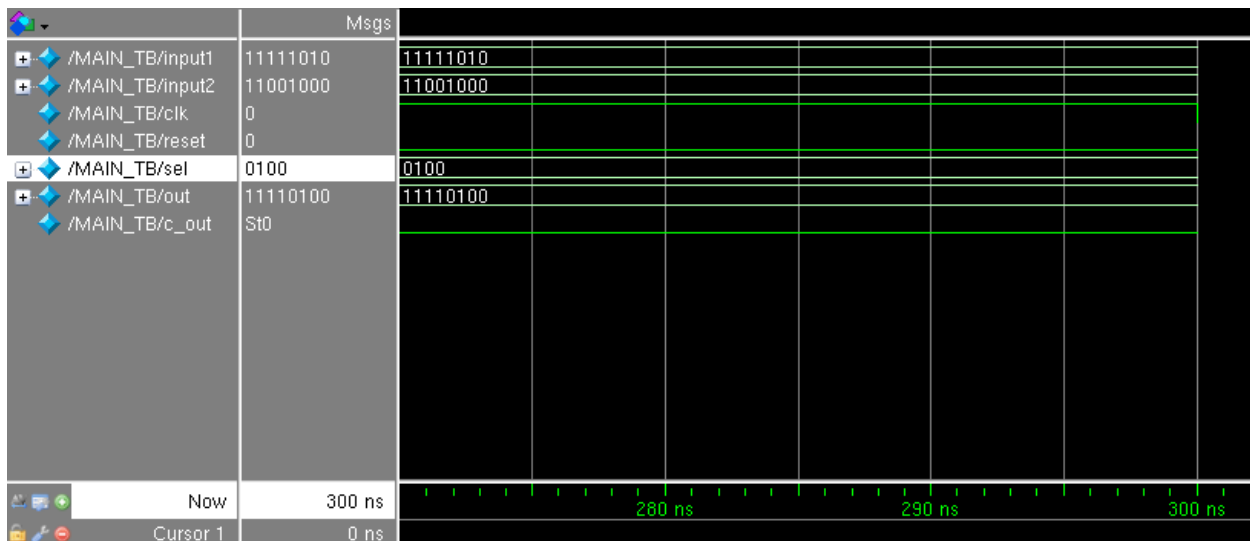

## Shift right:

input 1: (250)=11111010

input 2: (200)=11001000


sel: (0101)

reset : 0

clk : 1

out :input1>>1=0111101

c\_out: 0

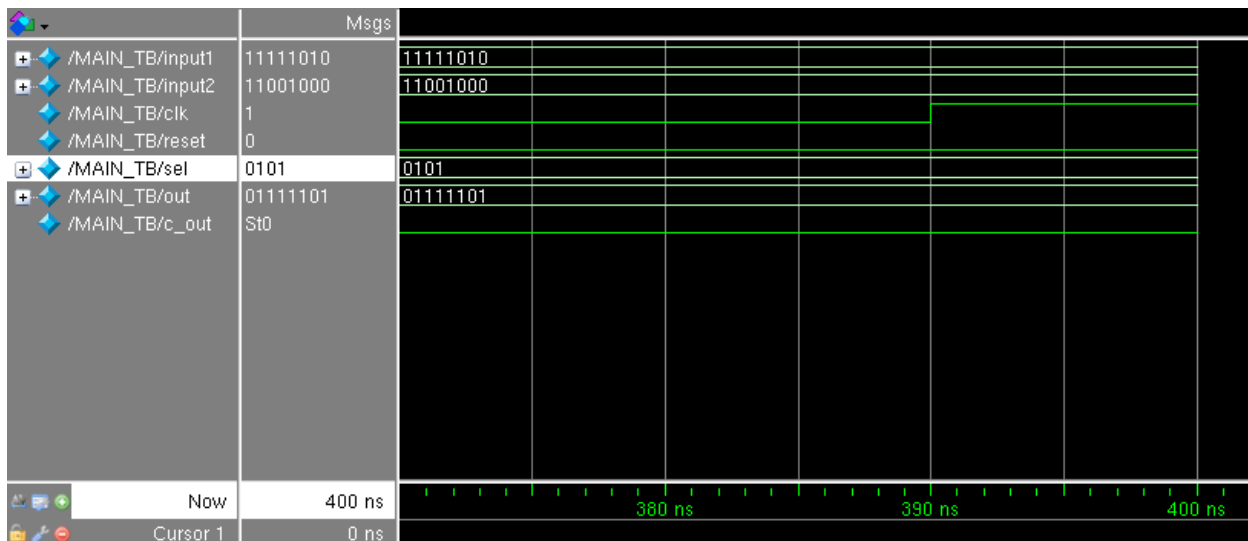

## Comparision :

input 1: (250)=11111010

input 2: (200)=11001000


sel: (0110) for greater than

reset : 0

clk : 1

out :input1>input2=00000000

c\_out: 1

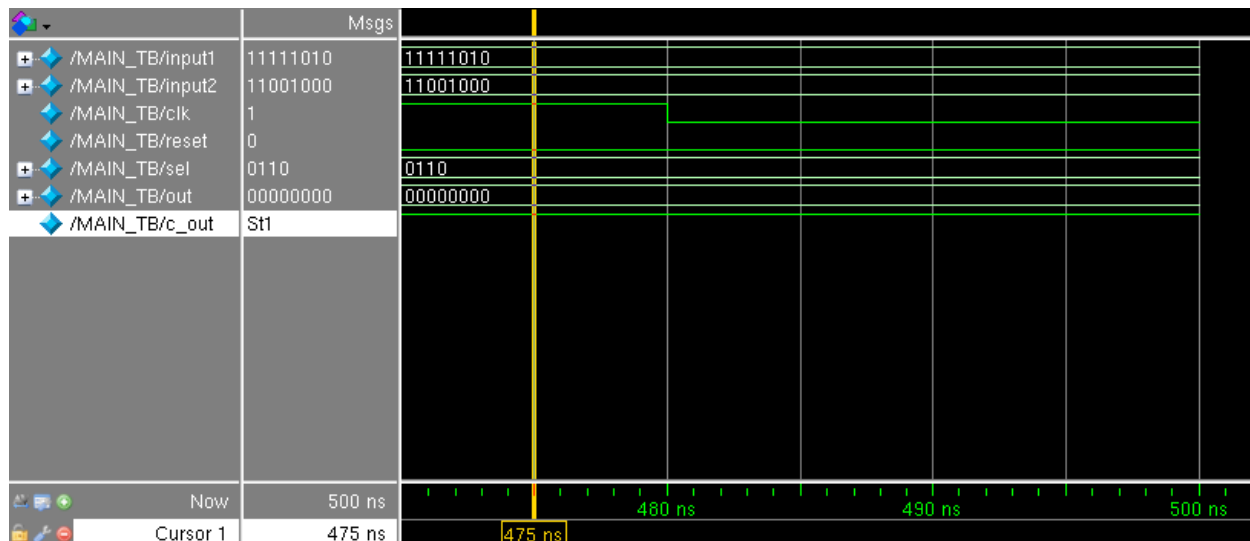

**Lesser than:**

input 1: (250)=11111010

input 2: (200)=11001000


sel: (0111) for lesser than

reset : 0

clk : 1

out :input1<input2=00000000

c\_out: 0

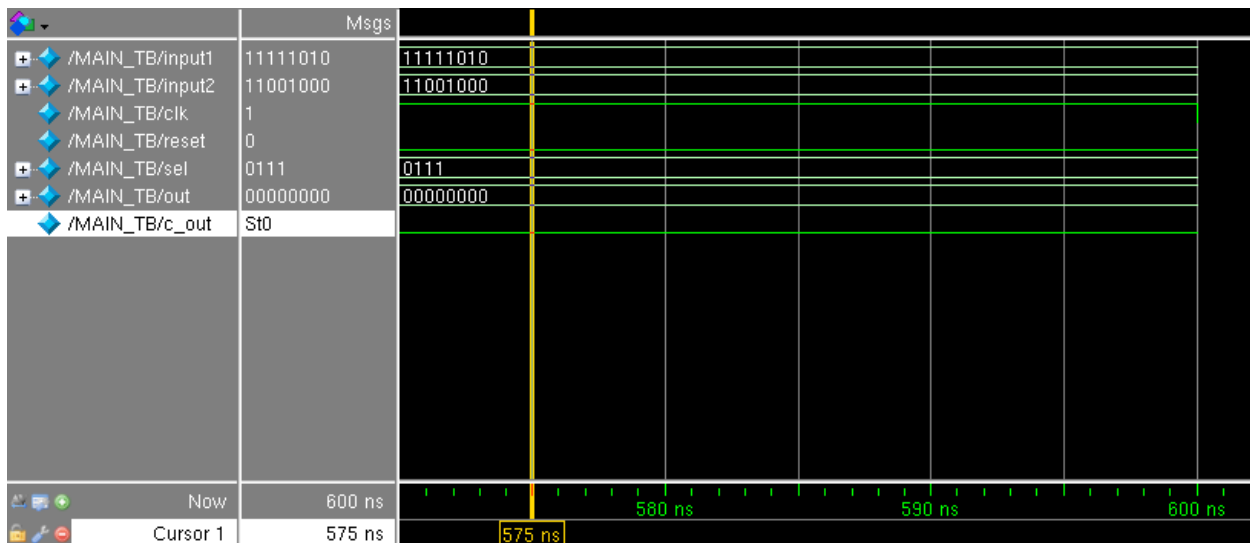

## Equality:

input 1: (250)=11111010

input 2: (200)=11001000

sel: (1000)

reset : 0

clk : 0

out :input1==input2=00000000

c\_out: 0

